

	Aufbau mit Schützen	Schaltzeichen	Wahrheitstabelle	Formel															
Schaltverstärker			<table border="1"> <thead> <tr> <th>S1</th> <th>H1</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> </tr> </tbody> </table>	S1	H1	1	1	0	0	$H1 = S1$									
S1	H1																		
1	1																		
0	0																		
Negator			<table border="1"> <thead> <tr> <th>S1</th> <th>H1</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> </tr> </tbody> </table>	S1	H1	1	0	0	1	$H1 = \overline{S1}$									
S1	H1																		
1	0																		
0	1																		
And			<table border="1"> <thead> <tr> <th>S1</th> <th>S2</th> <th>H1</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	S1	S2	H1	0	0	0	0	1	0	1	0	0	1	1	1	$H1 = S1 \wedge S2$
S1	S2	H1																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
NAnd			<table border="1"> <thead> <tr> <th>S1</th> <th>S2</th> <th>H1</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	S1	S2	H1	0	0	1	0	1	1	1	0	1	1	1	0	$H1 = \overline{S1 \wedge S2}$
S1	S2	H1																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
Or			<table border="1"> <thead> <tr> <th>S1</th> <th>S2</th> <th>H1</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	S1	S2	H1	0	0	0	0	1	1	1	0	1	1	1	1	$H1 = S1 \vee S2$
S1	S2	H1																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	
NOr			<table border="1"> <thead> <tr> <th>S1</th> <th>S2</th> <th>H1</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	S1	S2	H1	0	0	1	0	1	0	1	0	0	1	1	0	$H1 = \overline{S1 \vee S2}$
S1	S2	H1																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	

