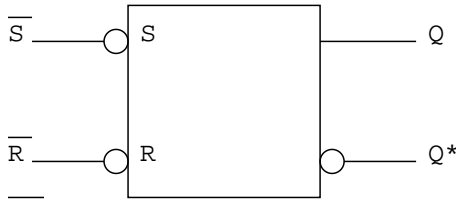
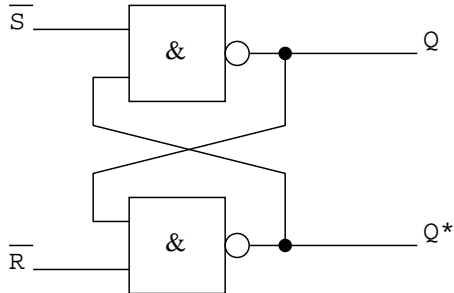
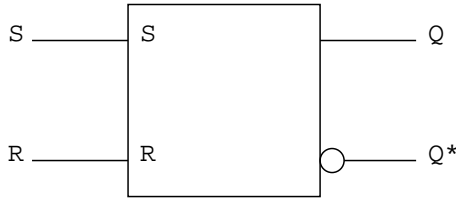
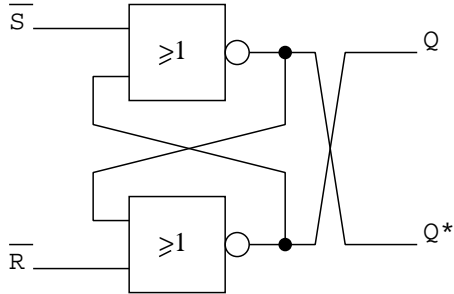
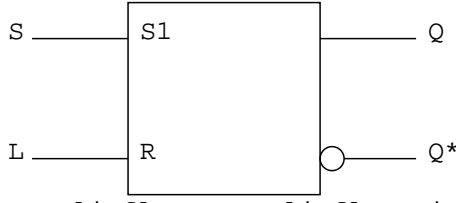
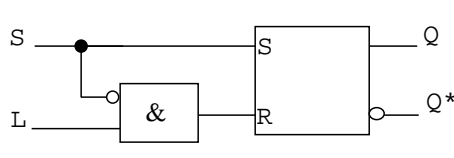
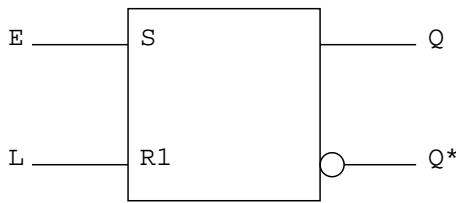
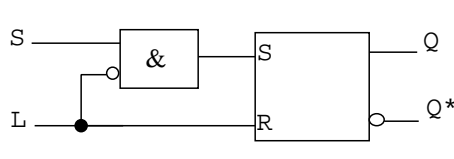
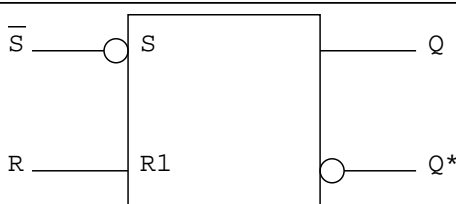
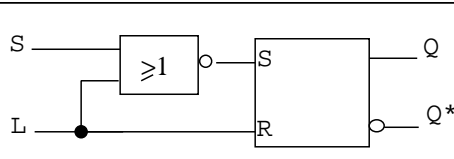


Schaltzeichen	Realisierung	Wertetabelle																				
 <p>RS-Flipflop</p>		<table border="1"> <thead> <tr> <th>S</th> <th>R</th> <th>Q</th> <th>Q*</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>*</td> <td>*</td> </tr> </tbody> </table>	S	R	Q	Q*	0	0	1	1	0	1	1	0	1	0	0	1	1	1	*	*
S	R	Q	Q*																			
0	0	1	1																			
0	1	1	0																			
1	0	0	1																			
1	1	*	*																			
 <p>RS-Flipflop</p>		<table border="1"> <thead> <tr> <th>S</th> <th>R</th> <th>Q</th> <th>Q*</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>*</td> <td>*</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	S	R	Q	Q*	0	0	*	*	0	1	0	1	1	0	1	0	1	1	0	0
S	R	Q	Q*																			
0	0	*	*																			
0	1	0	1																			
1	0	1	0																			
1	1	0	0																			
 <p>SL-Flipflop, RS-Flipflop mit dominierendem S-Eingang</p>		<table border="1"> <thead> <tr> <th>S</th> <th>L</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>*</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	S	L	Q	0	0	*	0	1	0	1	0	1	1	1	1					
S	L	Q																				
0	0	*																				
0	1	0																				
1	0	1																				
1	1	1																				
 <p>EL-Flipflop, RS-Flipflop mit dominierendem R-Eingang</p>		<table border="1"> <thead> <tr> <th>S</th> <th>L</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>*</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	S	L	Q	0	0	*	0	1	0	1	0	1	1	1	0					
S	L	Q																				
0	0	*																				
0	1	0																				
1	0	1																				
1	1	0																				
 <p>RS-Flipflop mit dominierendem R-Eingang</p>		<table border="1"> <thead> <tr> <th>S</th> <th>L</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>*</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	S	L	Q	0	0	1	0	1	0	1	0	*	1	1	0					
S	L	Q																				
0	0	1																				
0	1	0																				
1	0	*																				
1	1	0																				

A//